
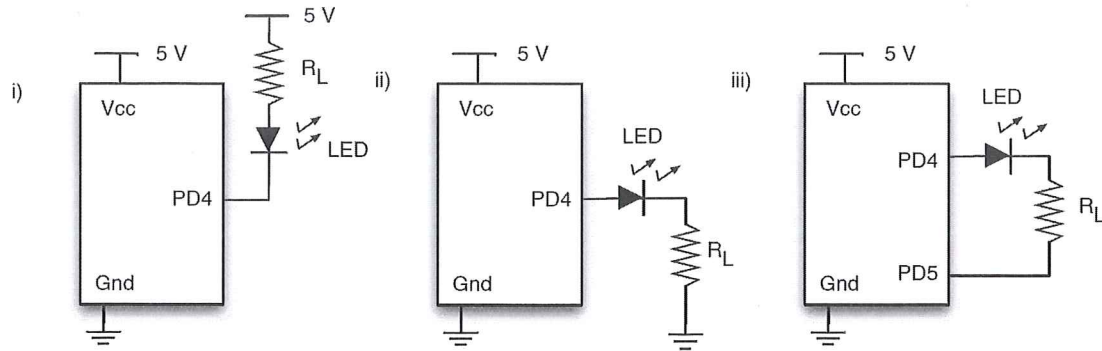


ENCE260 Embedded Systems tutorial 2 solutions

Q1

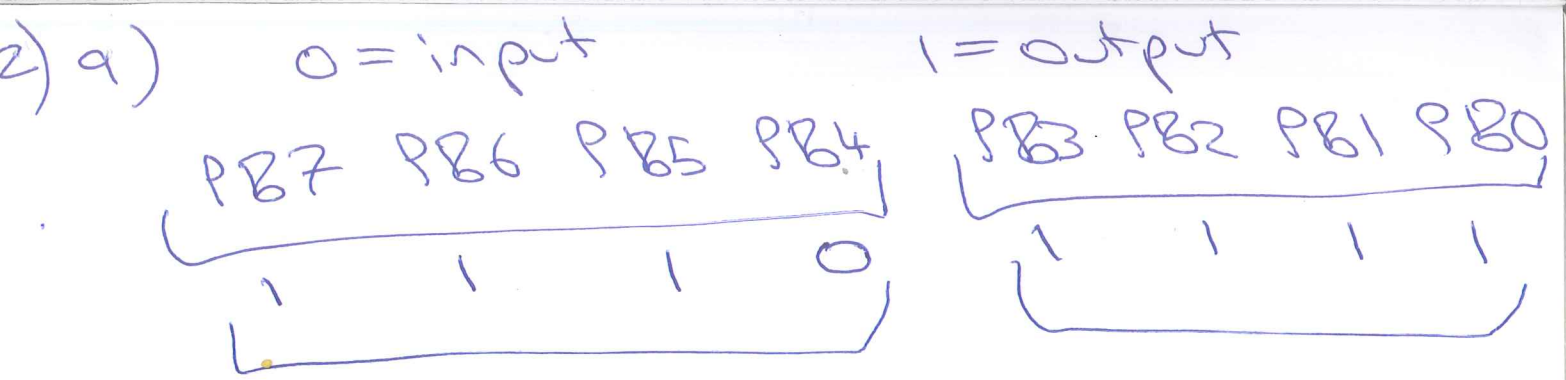

The resistor R_L in each case controls the current & hence luminance of the LED.



0xEF

b) L6 & L7

c) R3 is a guard resistor in case PB4 is accidentally set as a high output.

d) There is no pull-up resistor to 5V, for when the switch is not pushed.

e) $\text{PORTB} \&= \sim(1 \ll 7);$


f) PB0 = 1, PB2 = 0, PB3 = 0 (L1 & L3 on)

PB1 = 0 (L2 & L4 off)

PB6 = 1, PB7 = 1 (L6 & L7 off)

PB5 = 0 (L5 off)

PB4 does not matter as input

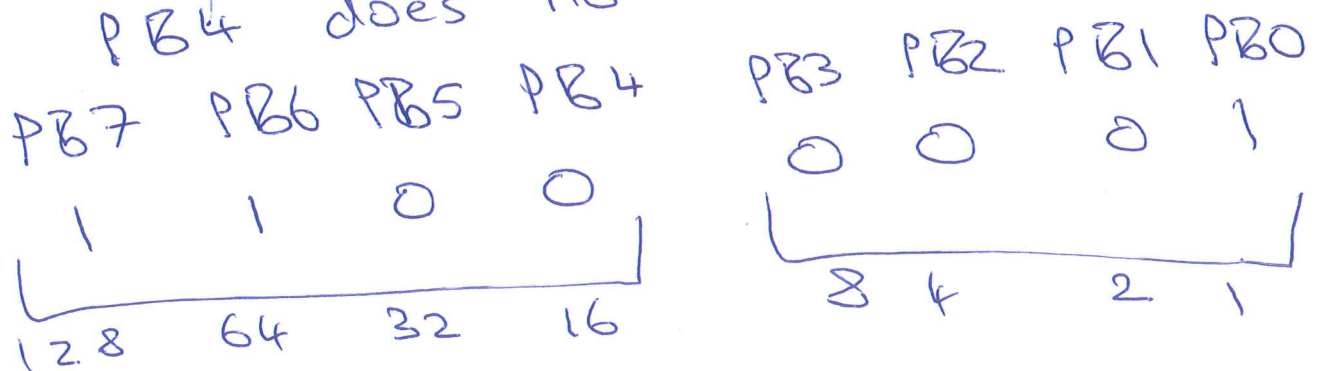

decimal value = $128 + 64 + 1 = 193$

3) a) 10

b) #define HUEY 10
#define DEWEY 400
#define LOUIE 10

flasher (HUEY, DEWEY, LOUIE);

$$c) \text{ Duty-cycle} = \frac{\text{ON_TIME}}{\text{ON_TIME} + \text{OFF_TIME}}$$

This will vary!

$$\text{Duty-cycle} = \frac{\text{HUEY}}{\text{DEWEY} - \text{LOUIE} + \text{HUEY}}$$

$$\text{Max Duty-cycle} = \frac{10}{400 - 9 + 10} = \frac{10}{401} \\ = 2.49 \%$$

$$\text{min Duty-cycle} = \frac{10}{400 - 0 + 10} = \frac{10}{410} = \frac{1}{41} \\ = 2.44 \%$$

d) Data abstraction allows routines to be used independently of the architecture.